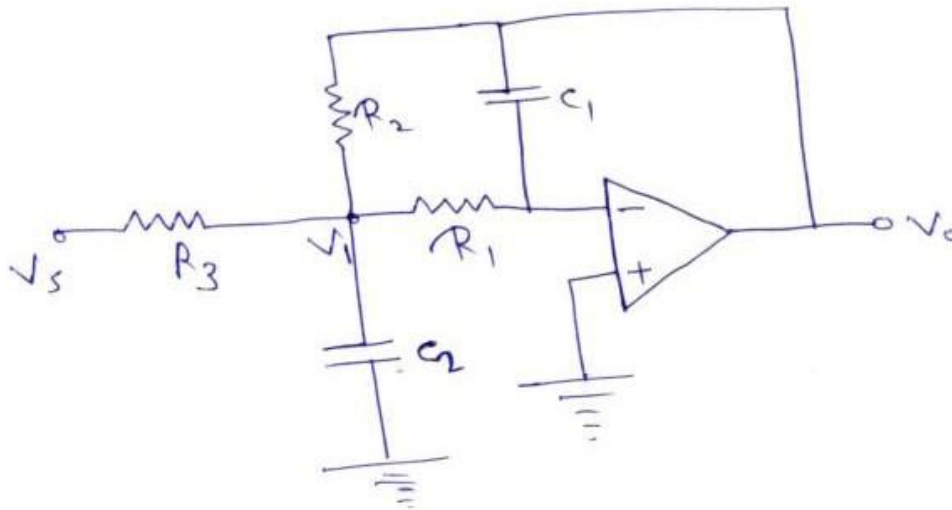


Question:

For the circuit shown,

- The damping factor ( $\xi$ ).
- The natural frequency ( $\omega_n$ ) in rad/sec.



For ,  $R_1 = R_2 = R_3 = 1 \text{ K}\Omega$

$C_1 = C_2 = 4 \mu\text{F}$

Note : Give your answer upto two decimal place.