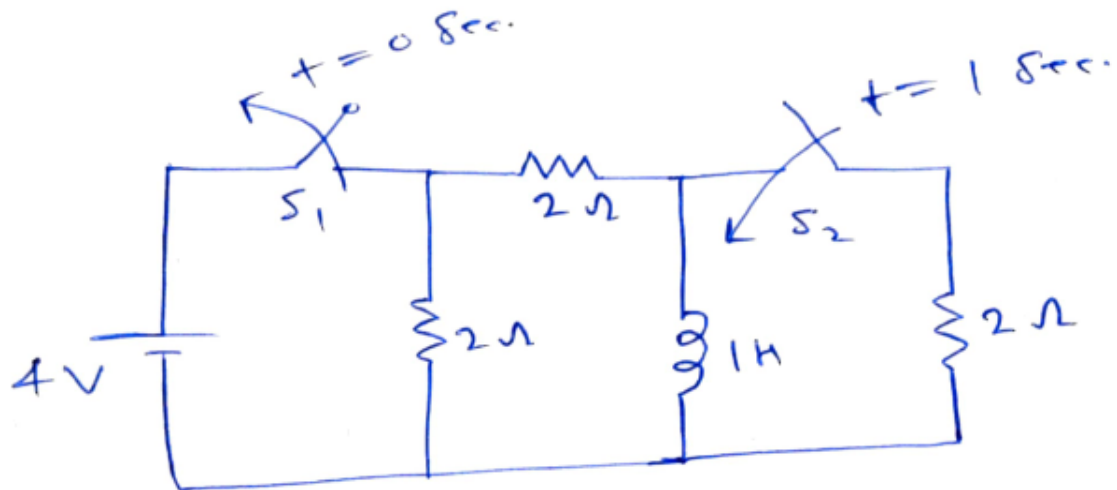


Q5 : Find the current through the inductor at:

a) $t = 1$ sec.

b) $t = 2$ sec, In the given network.



Note : Give your answer in amp and upto 3 decimal places.

--	--	--